

No.	Name	Application Sample	Circuit	Output	Remarks	Bridge Box DB-120A/350A
1	1-active-gage 2-wire system  Number of gages: 1	 Uniaxial stress (uniform tension/compression)		$e_o = \frac{E}{4} K_s \cdot \epsilon_o$ Ks: Gage factor $\epsilon_o$ : Strain E: Bridge voltage $e_o$ : Output voltage $R_g$ : Gage resistance R: Fixed resistance	Suitable for use under environment of less ambient temperature changes; no temperature compensation. x1 output	
2	1-active-gage 3-wire system  Number of gages: 1	 Uniaxial stress (uniform tension/compression)		$e_o = \frac{E}{4} K_s \cdot \epsilon_o$	No temperature compensation; thermal effect of leadwires cancelled. x1 output	
3	Dual 1-active-gage 2-wire system in series (to cancel bending strain)  Number of gages: 2	 Uniaxial stress (uniform tension/compression)		$e_o = \frac{E}{4} K_s \cdot \epsilon_o$ $R_{g1} \dots$ Strain: $\epsilon_1$ $R_{g2} \dots$ Strain: $\epsilon_2$ $\epsilon_o = \frac{\epsilon_1 + \epsilon_2}{2}$ R: Fixed resistance $R = R_{g1} + R_{g2}$	No temperature compensation; bending strain cancelled. x1 output	
4	Dual 1-active-gage 3-wire system in series (to cancel bending strain)  Number of gages: 2	 Uniaxial stress (uniform tension/compression)		$e_o = \frac{E}{4} K_s \cdot \epsilon_o$ $R_{g1} \dots$ Strain: $\epsilon_1$ $R_{g2} \dots$ Strain: $\epsilon_2$ $\epsilon_o = \frac{\epsilon_1 + \epsilon_2}{2}$ R: Fixed resistance $R = R_{g1} + R_{g2}$	No temperature compensation; bending strain cancelled; thermal effect of leadwires cancelled. x1 output	
5	Active-dummy 2-gage system  Number of gages: 2	 Uniaxial stress (uniform tension/compression)		$e_o = \frac{E}{4} K_s \cdot \epsilon_o$ Ks: Gage factor $\epsilon_o$ : Strain E: Bridge voltage $e_o$ : Output voltage $R_{g1}$ : Strain: $\epsilon_o$ $R_{g2} \dots$ Strain: 0	Temperature compensation; thermal effect of leadwires cancelled. x1 output	
6	Orthogonal 2-active-gage system  Number of gages: 2	 Uniaxial stress (uniform tension/compression)		$e_o = \frac{(1 + \nu) E}{4} K_s \cdot \epsilon_o$ $\nu$ : Poisson's ratio $R_{g1}, R_{g2}$ : Gage resistance $R_{g1} \dots$ Strain: $\epsilon_o$ $R_{g2} \dots$ Strain: $-\nu \epsilon_o$ R: Fixed resistance	Temperature compensation; thermal effect of leadwires cancelled. x(1+ $\nu$ ) output	
7	2-active-gage system (for bending strain measurement)  Number of gages: 2	 Bending stress		$e_o = \frac{E}{2} K_s \cdot \epsilon_o$ $R_{g1} \dots$ Strain: $\epsilon_o$ $R_{g2} \dots$ Strain: $-\epsilon_o$ R: Fixed resistance	Temperature compensation; thermal effect of leadwires cancelled; compressive/tensile strain cancelled. x2 output	
8	Opposite side 2-active-gage 2-wire system  Number of gages: 2	 Uniaxial stress (uniform tension/compression)		$e_o = \frac{E}{2} K_s \cdot \epsilon_o$ $R_{g1} \dots$ Strain: $\epsilon_o$ $R_{g2} \dots$ Strain: $\epsilon_o$ R: Fixed resistance	No temperature compensation; bending strain cancelled by bonding to the front and rear. x2 output	

No.	Name	Application Sample	Circuit	Output	Remarks	Bridge Box DB-120A/350A
9	Opposite side 2-active-gage 3-wire system  Number of gages: 2	 Uniaxial stress (uniform tension/compression)		$\epsilon_o = \frac{E}{2} K_s \cdot \epsilon_o$ $Rg_1, \dots$ Strain: $\epsilon_o$ $Rg_2, \dots$ Strain: $\epsilon_o$ $R$ : Fixed resistance	No temperature compensation; thermal effect of leadwires cancelled; bending strain cancelled by bonding to the front and rear. x2 output	
10	4-active-gage system (for bending strain measurement)  Number of gages: 4	 Bending stress		$\epsilon_o = K_s \cdot \epsilon_o \cdot E$ $Rg_1, Rg_3, \dots$ Bending strain: $\epsilon_o$ $Rg_2, Rg_4, \dots$ Bending strain: $-\epsilon_o$	Temperature compensation; thermal effect of leadwires cancelled; compressive/tensile strain cancelled. x4 output	
11	Orthogonal 4-active-gage system  Number of gages: 4	 Uniaxial stress (uniform tension/compression)		$\epsilon_o = \frac{(1 + \nu) E}{2} K_s \cdot \epsilon_o$ $\nu$ : Poisson's ratio $Rg_1, Rg_3, \dots$ Strain: $\epsilon_o$ $Rg_2, Rg_4, \dots$ Strain: $-\nu \epsilon_o$	Temperature compensation; thermal effect of leadwires cancelled. x2(1+ν) output	
12	Active-dummy 4-gage system  Number of gages: 4	 Uniaxial stress (uniform tension/compression) Active gages Dummy gages		$\epsilon_o = \frac{E}{2} K_s \cdot \epsilon_o$ $Rg_1, Rg_3, \dots$ Strain: $\epsilon_o$ $Rg_2, Rg_4, \dots$ Strain: 0	Temperature compensation; thermal effect of leadwires cancelled; bending strain cancelled by bonding to the front and rear. x2 output	
13	2-active-gage system (for bending strain measurement)  Number of gages: 2			$\epsilon_o = \frac{E}{2} K_s \cdot \epsilon_o$ $Rg_1, \dots$ Bending strain: $\epsilon_o$ $Rg_2, \dots$ Bending strain: $-\epsilon_o$ $R$ : Fixed resistance	Temperature compensation; thermal effect of leadwires cancelled. x2 output	
14	4-active-gage system (for bending strain measurement)  Number of gages: 4			$\epsilon_o = K_s \cdot \epsilon_o \cdot E$ $Rg_1, Rg_3, \dots$ Bending strain: $\epsilon_o$ $Rg_2, Rg_4, \dots$ Bending strain: $-\epsilon_o$	Temperature compensation; thermal effect of leadwires cancelled. x4 output	
15	4-active-1-gage system (for mean strain measurement)  Number of gages: 4			$\epsilon_o = \frac{E}{2} K_s \cdot \epsilon_o$ $\epsilon_o = \frac{\epsilon_1 + \epsilon_2 + \epsilon_3 + \epsilon_4}{4}$ $R$ : Fixed resistance $Rg = R$ $R = Rg_1 = Rg_2 = Rg_3 = Rg_4$	No temperature compensation; mean strain. x1 output	

●Relation between strain and voltage

The output of a strain-gage bridge is expressed as a strain quantity ( $\mu\epsilon$ ) or an output voltage (mV/V or  $\mu\text{V/V}$ ) against the bridge voltage. The strain quantity and the output voltage have the following relation:

$$\epsilon_o = \frac{E}{4} K_s \cdot \epsilon_o$$

If the bridge voltage  $E = 1\text{V}$  and the gage factor  $K_s = 2.00$ ,

$$2\epsilon_o = \epsilon_o.$$

Thus, a strain output is always 2 times larger than a bridge output voltage.

$$\text{e.g. } 3000\mu\epsilon \rightarrow 1500\mu\text{V/V} = 1.5\text{mV/V}$$